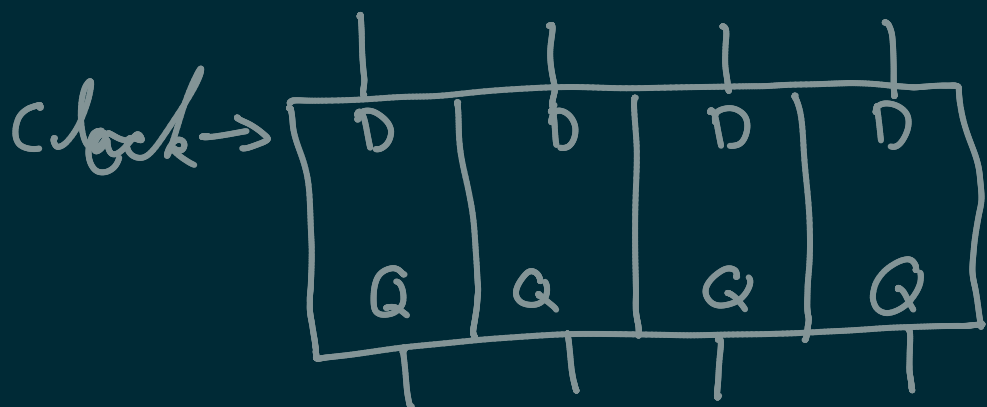


Register



Flip flop = 1 bit memory cell

Register = group of n register


4 bit register : 4 flipflops : 4 bits word



SRAM Multiplexer

  


Tri-State buffer

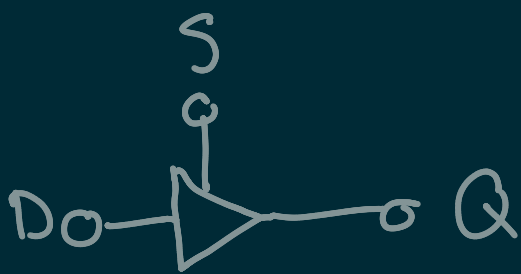

S	Q
0	Z (High Impedance)
1	D


SRAM Multiplexer with tri-state buffers

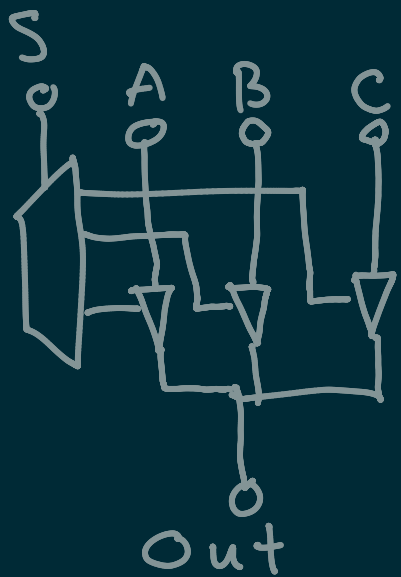

Only one tri-state buffer must be active at a time (otherwise short-circuit)

SRAM Decoder

Linear array :

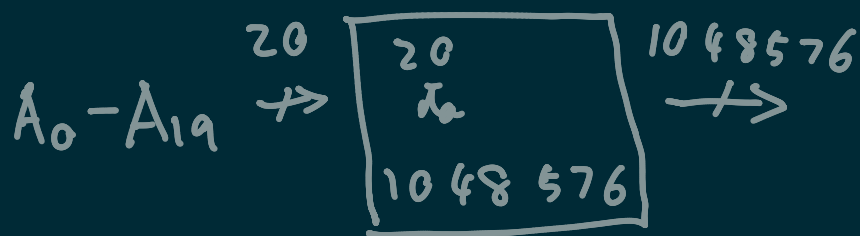

1048576 D flip flop and Tri-state buffers




1-bit output


Rectangle array :

Row decoder

A10 - A19

 


1048576 D flip flop in 1024 x 1024 grid

 

Column decoder

A0 - A10

 

0 1023

