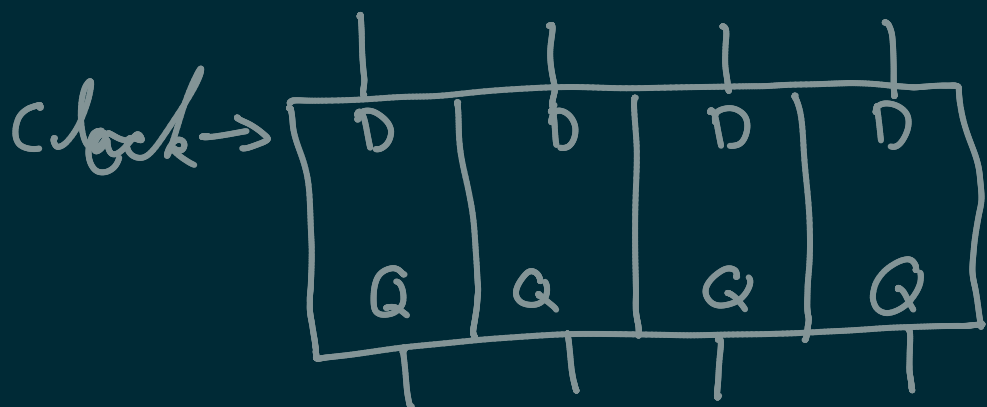


# Register



Flip flop = 1 bit memory cell

Register = group of  $n$  register


4 bit register : 4 flipflops : 4 bits word



## SRAM Multiplexer

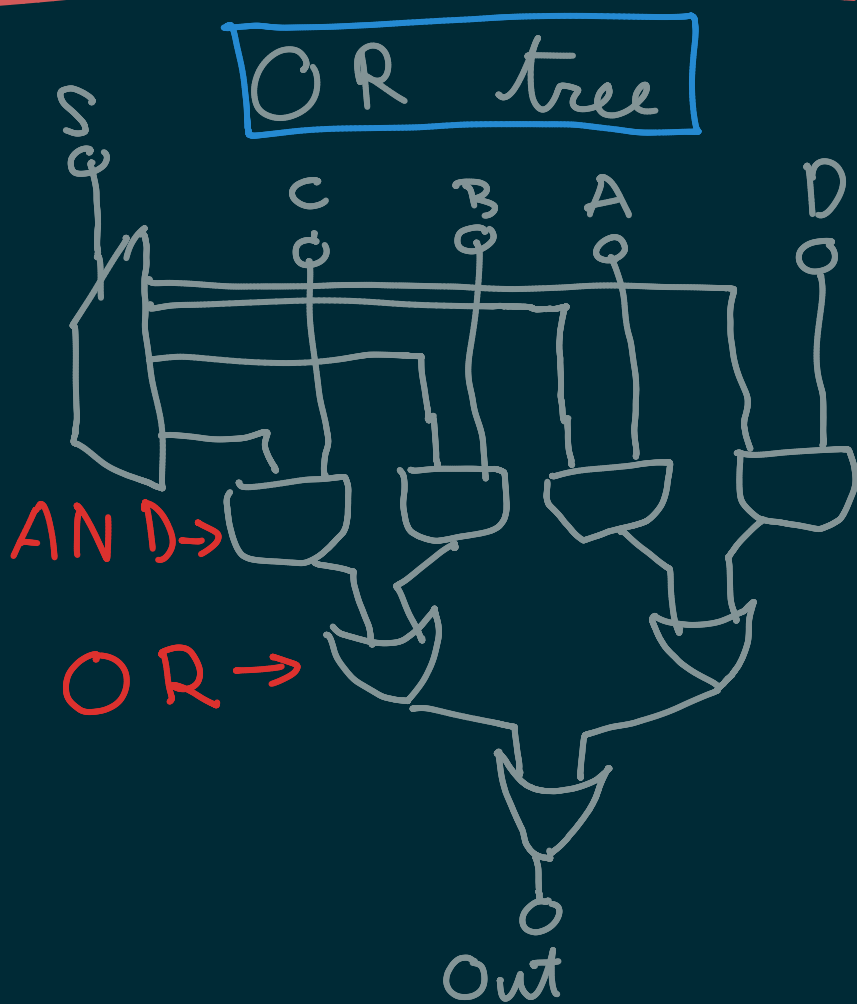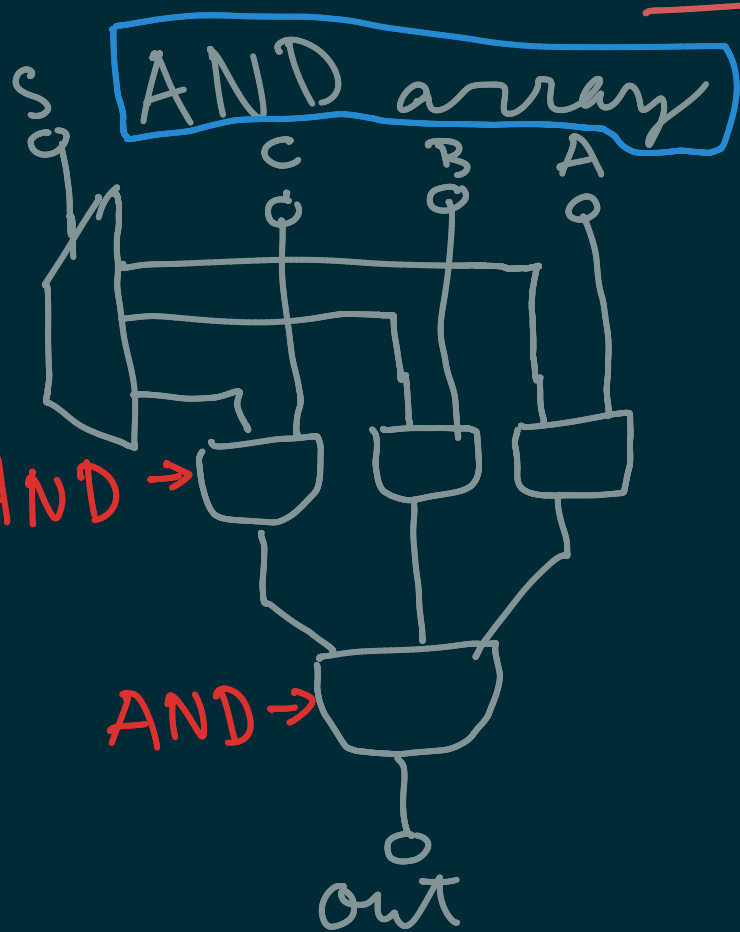


# Tri-State buffer

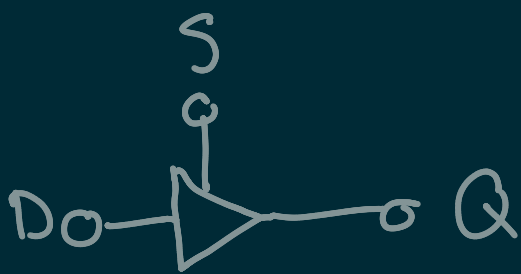

S	Q
0	Z (High Impedance)
1	D

 
## SRAM Multiplexer with tri-state buffers



Only one tri-state buffer must be active at a time (otherwise short-circuit)

## SRAM Decoder

Linear array :

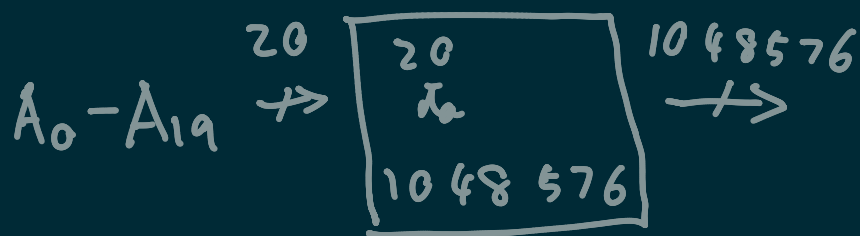

1048576 D flip flop and Tri-state buffers




1-bit output


Rectangle array :

Row decoder

A10 - A19

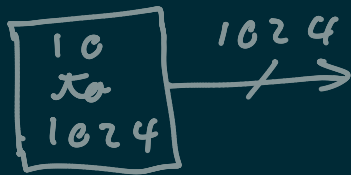


1048576 D flip flop in 1024 x 1024 grid

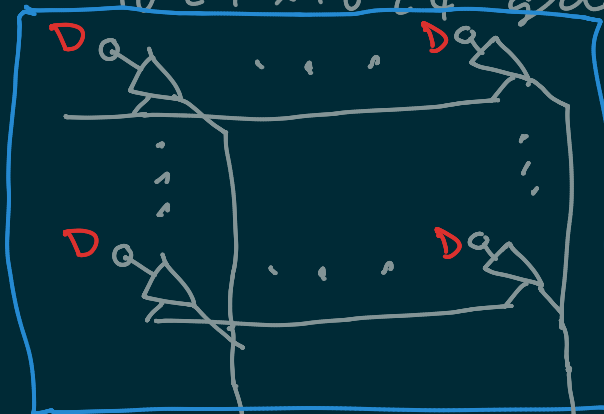

Column decoder

A0 - A10

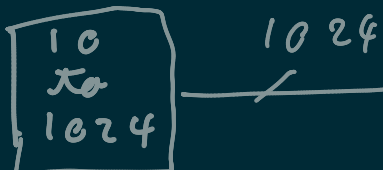

0 1023

